

**FYSE302 Electronics 1B**  
**Final Exam 11.5.2012**

1. Briefly explain/describe:
  - (a) Common mode rejection ratio (CMRR) (1p)
  - (b) Half-wave and full-wave rectification (1p)
  - (c) Zener diode, and how it can be used in voltage regulation (2p)
  - (d) Negative and positive feedback. Draw also the block diagrams (2p)
2. Consider the RCL-circuit shown in figure 1. Determine the resonance frequency  $\omega_0$ , i.e. the frequency when the total impedance of the circuit is purely real. What is the total impedance at the resonance?

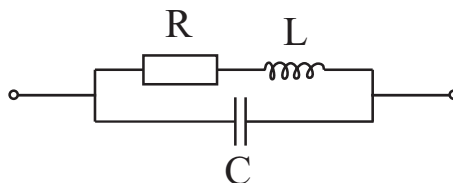


Figure 1:

3. The input resistance  $R_{in}$  of a voltage amplifier needs to be as high as possible, so that the amplifier does not induce much load on the other circuitry. A simple inverting amplifier circuit shown in figure 2a) is not an ideal choice in this sense.
  - (a) What is the highest possible input impedance  $R_{in} = V_i/I_i$  for the circuit of figure 2a), if the gain  $V_o/V_i$  needs to be  $-100$  and resistors higher than  $1\text{ M}\Omega$  are not allowed to use.
  - (b) Better circuit is shown in figure 2b). Choose the components so that the gain  $V_o/V_i = -100$  and the input impedance  $R_{in} = V_i/I_i = 1\text{ M}\Omega$ . Largest resistor allowed is  $1\text{ M}\Omega$ . (Resistors larger than  $1\text{ M}\Omega$  usually induce problems)


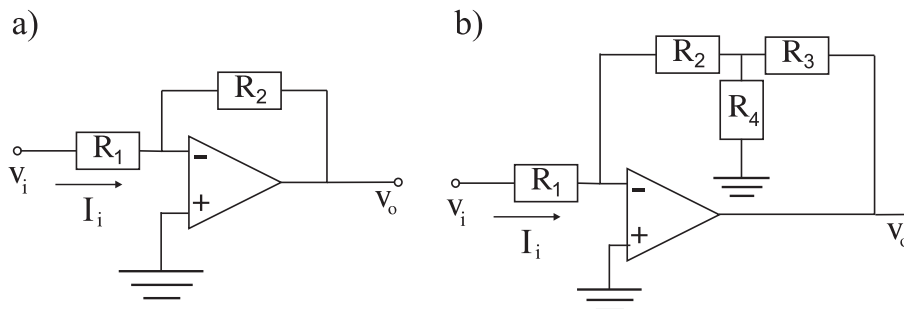



Figure 2:

4. Figure on right represents a self-biased circuit for a bipolar transistor. Choose the values for  $R_C$ ,  $R_1$  and  $R_2$  in such a way that the operation point becomes  $I_C = 1.25$  mA and  $V_{CE} = 5$  V. Choose  $R_E = 2$  k $\Omega$  and  $V_{CC} = 15$  V. For the silicon transistor in question  $\beta = 100$  and  $I_{CBO} \approx 0$  A. Now  $R_1$  and  $R_2$  have to be chosen so that  $\beta \gg R_B/R_E \gg 1$ , where  $R_B = R_1 || R_2$ . Why? In calculations choose  $R_B/R_E = 10$ .

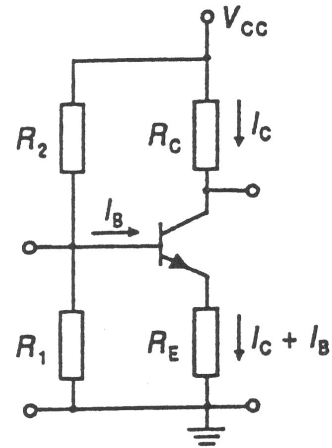

5. In figure 3a) there is shown an amplifier circuit based on a npn-transistor and figure 3b) illustrates its small-signal model.
- (a) Explain what is the small-signal model and what is it used for. What is described by the symbols ( $r_\pi$ ,  $C_\pi$ , etc.) in figure 3b)? Is there anything missing?
- (b) Determine the gain of the system  $A = V_O/V_S$  at low frequencies ( $C_{C1}$  ja  $C_{C2}$  more significant than the other capacitances) assuming  $R_B \gg r_\pi$ . Explain qualitatively what happens at very high frequencies and at middle frequencies.

a)

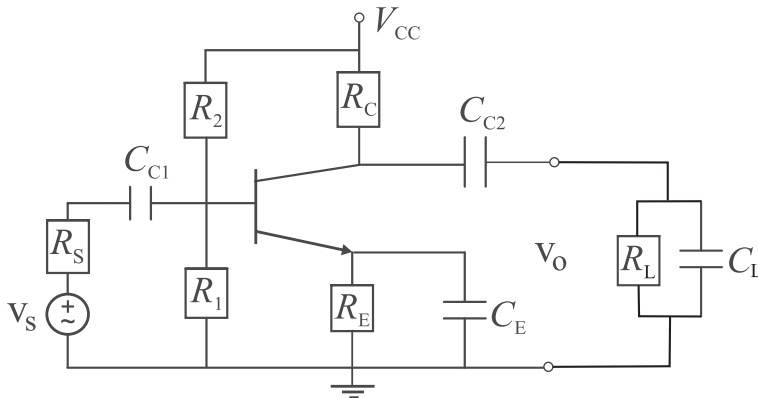

b)

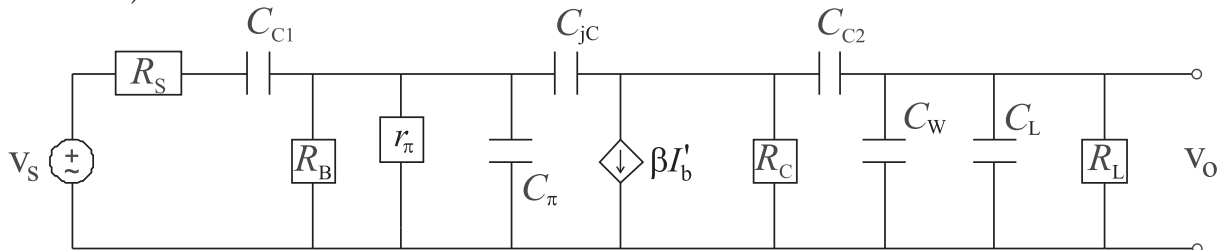


Figure 3: