

FYSE302 Electronics I (part B)

Final exam 21.5.2010

Lecturer: Arto Javanainen

1. Briefly define/explain:
 - a. Root-mean-square value (RMS) (1 p.)
 - b. Series resonance (1 p.)
 - c. Half- and full-wave rectification (1 p.)
 - d. Dynamic range of an amplifier (1 p.)
 - e. Active high-pass filter based on an operational amplifier (Draw a circuit and sketch the Bode plot for the magnitude of the transfer function). (2p)

2. Define the transfer function v_o/v_s as a function of frequency for the circuit in figure 1, where v_o and v_s are the complex amplitudes for the voltages across the resistance [$v_o(t)$] and the signal generator [$v_s(t) = V_m \cos(\omega t)$], respectively. Draw the Bode plots for both the magnitude and the phase, when $L = 200$ mH and $R = 500 \Omega$. For what the circuit can be used for?

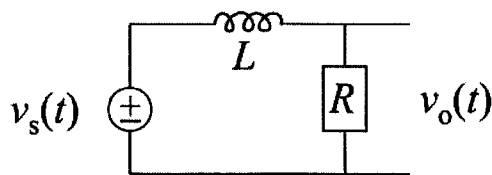


figure 1.

3. Define the transfer function U_2/E for the circuit in figure 2. $R_2 = 9R_1$, $R_1 = 1 \Omega$, $R = 1 \Omega$, $C = 1$ F.

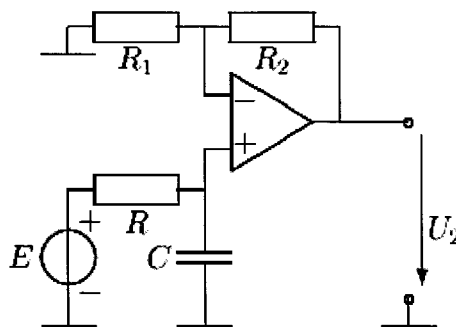


figure 2.

Turn the page!

4. Define a) the operation point (collector current I_C and collector-to-emitter voltage V_{CE}) and b) the AC-voltage amplification at center-frequency range for the common-emitter amplifier in figure 3. What determines the amplification? Typical values for the transistor parameters are: $h_{fe} \approx \beta = 250$, $h_{ie} \approx r_{\pi} = 5 \text{ k}\Omega$, $V_{BE} = 0,7 \text{ V}$.

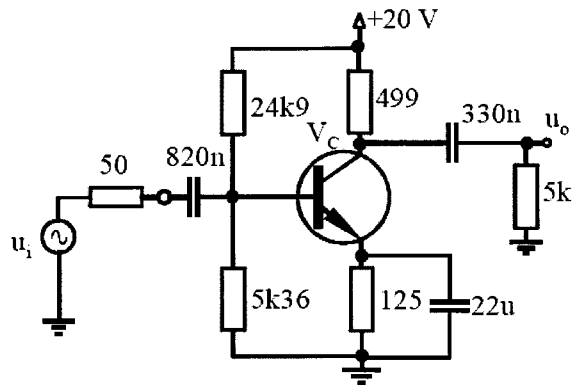


figure 3.

5. The system is represented by the following equations:

$$\begin{aligned} V_5 &= BV_3 \\ V_2 &= V_1 - V_4 \\ V_3 &= AV_2 \\ V_4 &= CV_3, \end{aligned}$$

where A, B and C are the transfer functions for the different blocks in the system and V_i 's are the signals at different points in the system. Draw the block diagram and define the total transfer function $G_{TOT} = V_5/V_1$ for the whole system.