

FYSE302 Electronics 1B
Final Exam 27.5.2011

1. Briefly explain/describe:
 - (a) Dynamic resistance (2p)
 - (b) Common mode rejection ratio (2p)
 - (c) DA conversion (2p)
2. At the circuit shown in figure 1 $v_s(t) = 10\sqrt{2} \cos(\omega t)$ V. Determine the current flowing through the coil by using thévenin's theorem, when $\omega = 900$ Hz.

 


Figure 1:

3. The input resistance R_{in} of a voltage amplifier needs to be as high as possible, so that the amplifier does not induce much load on the other circuitry. A simple inverting amplifier circuit shown in figure 2(a) is not an ideal choice in this sense.
 - (a) What is the highest possible input impedance $R_{in} = V_i/I_i$ for the circuit of figure 2(a), if the gain V_o/V_i needs to be -100 and resistors higher than $1 \text{ M}\Omega$ are not allowed to use.
 - (b) Better circuit is shown in figure 2(b). Choose the components so that the gain $V_o/V_i = -100$ and the input impedance $R_{in} = V_i/I_i = 1 \text{ M}\Omega$. Largest resistor allowed is $1 \text{ M}\Omega$. (Resistors larger than $1 \text{ M}\Omega$ usually induce problems)

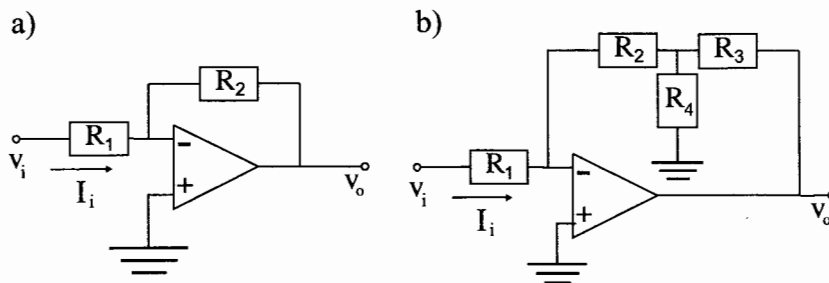


Figure 2:

4. The circuit presented in figure 3 is used as a power amplifier. The current amplification factor of a silicon transistor is $\beta = 100$. Furthermore, $V_{CC} = 15$ V, $R_1 = 10$ k Ω and $R_2 = 30$ k Ω

- (a) Choose R_E and R_C in such a way that the operation point of the transistor becomes $V_{CE} = 6$ V ja $I_C = 2$ mA.
 (b) Sketch the $i_C - v_{CE}$ -curves and draw the dc load-line in the same figure.

Draw the ac load-line when $R_L = 3$ k Ω . Find out the ac-component of the output voltage v_o , when the input signal at the base is $i_b = 10 \sin(\omega t)$ μ A.

 


Figure 3:

5. Lets consider the circuit shown in Fig. 4, where $R_L = 8$ k Ω and $V_{GG} = 2$ V, and the values for the parameters describing the small-signal model of depletion field-effect MOSFET -transistor are $I_{DSS} = 10$ mA, $g_{m0} = 5000$ μ S ja $r_d = 50$ k Ω . Determine I_D and choose V_{DD} so, that at the operation point $V_{DS} = 8$ V. Calculate the voltage amplification $|v_o/v_s|$ at this operation point using the small-signal model. Here v_s and v_o are the complex amplitudes of the small signals. For a MOSFET:

$$i_D = I_{DSS} \left(1 - \frac{v_{gs}}{V_P} \right)^2, \quad g_m = \frac{di_D}{dv_{GS}}$$

$$\text{and } g_{m0} = \left. \frac{di_D}{dv_{GS}} \right|_{v_{GS}=0}$$


 


Figure 4:

PN2222

General Purpose Transistor

 

TO-92
1. Emitter 2. Base 3. Collector

NPN Epitaxial Silicon Transistor

Absolute Maximum Ratings $T_a=25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Value	Units
V_{CBO}	Collector-Base Voltage	60	V
V_{CEO}	Collector-Emitter Voltage	30	V
V_{EBO}	Emitter-Base Voltage	5	V
I_C	Collector Current	600	mA
P_C	Collector Power Dissipation	625	mW
T_J	Junction Temperature	150	$^\circ\text{C}$
T_{STG}	Storage Temperature	-55 ~ 150	$^\circ\text{C}$

Electrical Characteristics $T_a=25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Test Condition	Min.	Max.	Units
BV_{CBO}	Collector-Base Breakdown Voltage	$I_C=10\mu\text{A}, I_E=0$	60		V
BV_{CEO}	Collector Emitter Breakdown Voltage	$I_C=10\text{mA}, I_B=0$	30		V
BV_{EBO}	Emitter-Base Breakdown Voltage	$I_E=10\mu\text{A}, I_C=0$	5		V
I_{CBO}	Collector Cut-off Current	$V_{CB}=50\text{V}, I_E=0$		0.01	μA
I_{EBO}	Emitter Cut-off Current	$V_{EB}=3\text{V}, I_C=0$		10	nA
h_{FE}	DC Current Gain	$V_{CE}=10\text{V}, I_C=0.1\text{mA}$ $V_{CE}=10\text{V}, *I_C=150\text{mA}$	35 100	300	
$V_{CE}(\text{sat})$	* Collector-Emitter Saturation Voltage	$I_C=500\text{mA}, I_B=50\text{mA}$		1	V
$V_{BE}(\text{sat})$	* Base-Emitter Saturation Voltage	$I_C=500\text{mA}, I_B=50\text{mA}$		2	V
f_T	Current Gain Bandwidth Product	$V_{CE}=20\text{V}, I_C=20\text{mA}, f=100\text{MHz}$	300		MHz
C_{ob}	Output Capacitance	$V_{CB}=10\text{V}, I_E=0, f=1\text{MHz}$		8	pF

* Pulse Test: Pulse Width $\leq 300\mu\text{s}$, Duty Cycle $\leq 2\%$