 


FYSE420 DIGITAL ELECTRONICS

02.07.2010

K.Loberg

1. In picture given below show output sequence of asynchronous circuit. Design circuit and give an **excitation functions**, **transition table** and **total state table** for an asynchronous circuit. Underscore the stable states in transition table. Avoid hazards and remember a proper binary state assignment. X is input, Z0 and Z1 are outputs. Use only gates.



2. Explain shortly
 - (a) Mealy state machine. Draw simple block diagram.
 - (b) Moore state machine. Draw simple block diagram.
 - (c) One-Hot Encoded state machine.
 - (d) Registered-Output Finite State Machine
 - (e) What kind of problems we have in Asynchronous Sequential Circuits.

3. Give a circuit diagram of the VHDL description shown below.

```
entity comblog is port(
    sel : in integer range 0 to 3;
    x,y, z : in std_logic;
    res : out std_logic);
end entity comblog;

architecture behavior_arch of comblog is
begin
    case sel is
        when 0 => res <= x and y;
        when 1 => res <= y xor z;
        when 2 => res <= x nand z;
        when others => res <= x nor z;
    end case;
end process;
end architecture behavior_arch;
```

4. Give the circuit diagram of the VHDL description shown below. Assume that you have positive edge triggered D flip-flops, which has also Clock Enable (CE) input. CE is active on level -1-.

```
library IEEE;
use ieee.std_logic_1164.all;
entity reg is
port (
    ina : in std_logic_vector(7 downto 0);
    enable : in std_logic;
    clk,start: in std_logic;
    com : out std_logic_vector(7 downto 0)
);
end reg;

architecture reg_arch of reg is
    signal reg_out : std_logic_vector(7 downto 0);
begin
    process (clk) is
    begin
        if (clk'event and clk = '1') then
            if enable = '1' then
                reg_out <= ina;
            end if;
        end if;
    end process;

    process(reg_out,start) is
        variable varcom : std_logic_vector(7 downto 0);
```

