

3. Anna kytkentäkaavio alla olevalle VHDL kuvaukselle.

```
entity comblog is port(  
    sel : in integer range 0 to 3;  
    x,y, z : in std_logic;  
    res : out std_logic);  
end entity comblog;  
  
architecture behavior_arch of comblog is  
begin  
    case sel is  
        when 0 => res <= x and y;  
        when 1 => res <= y xor z;  
        when 2 => res <= x nand z;  
        when others => res <= x nor z;  
    end case;  
    end process;  
end architecture behavior_arch;
```

4. Anna kytkentäkaavio alla olevalle VHDL kuvaukselle. Käytössäsi on D-ff, joka on nousevalla reunalla aktiivinen ja sillä on Clock Enable (CE) tulo. CE on ylätila-aktiivinen (level -1-) tulo.

```
library IEEE;  
use ieee.std_logic_1164.all;  
entity reg is  
port (  
    ina : in std_logic_vector(7 downto 0);  
    enable : in std_logic;  
    clk,start: in std_logic;  
    com : out std_logic_vector(7 downto 0)  
);  
end reg;  
  
architecture reg_arch of reg is  
    signal reg_out : std_logic_vector(7 downto 0);  
begin  
    process (clk) is  
        begin  
            if (clk'event and clk = '1') then  
                if enable = '1' then  
                    reg_out <= ina;  
                end if;  
            end if;  
        end process;  
  
        process(reg_out,start) is  
            variable varcom : std_logic_vector(7 downto 0);
```


```

begin
  if start = '0' then
    varcom := "00000000";
  else
    varcom := reg_out;
  end if;
  com <= varcom;
end process;
end architecture reg_arch ;

```

5. Anna kytkentäkaavio liitteessä olevalle VHDL-kuvaukselle. Esitä kytkentä kuvauksen mukaisella rakenteella. Mikä kytkentä on kyseessä?

 6. Design the synchronous **binary encoded** finite state machine (FSM). The external control input is *RUN*. If *RUN* = -1-, the FSM enters to the continuous sequence described below. When *RUN* goes to the -0- level, the FSM stop to the state where $A = B = -0-$. If outputs A or B are -1- when *RUN* goes to the level : $RUN=0$, the FSM sequence runs normally until $A = B = -0-$ at the same time. Let the first state be *a*, when outputs $A = -0-$ and $B = -0-$. Draw only clock connections between DFFs and give the boolean functions of the exitationfunctions of DFFs. Outputs A and B has own DFFs. The solution is Registered Output FSM, which has binary-encoded states.



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
-- Comments
--
```

```
-----
-- design for examination. By KL 03.05.2011 -----
-----
```

```
-- Comments ---
--
```

```
entity nandgate is
  port (a,b,c : in std_logic;
        y : out std_logic);
end nandgate;
```

```
architecture nandgate_arch of nandgate is
begin
  y <= not (a and b and c);
end nandgate_arch;
```

```
-----
-- Comments --
-----
```

```
--
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity notgate is
  port ( inport : in std_logic;
        outport : out std_logic);
end notgate;
```

```
architecture notgate_arch of notgate is
begin
  outport <= not inport;
end notgate_arch;
```

```
-----
-- Comments. --
-----
```

```
--
--
--
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```

entity tentti is
  port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : in STD_LOGIC;
        d0 : out STD_LOGIC;
        d1 : out STD_LOGIC;
        d2 : out STD_LOGIC;
        d3 : out STD_LOGIC;
        d4 : out STD_LOGIC;
        d5 : out STD_LOGIC;
        d6 : out STD_LOGIC;
        d7 : out STD_LOGIC);
end tentti;

```

```

architecture tentti_arch of tentti is
  component nandgate is
    port (a,b,c : in std_logic;
          y : out std_logic);
  end component;

  component notgate is
    port (inport : in std_logic;
          outport : out std_logic);
  end component;

  -- declare local signals : inva invb and invc --
  signal inva, invb, invc : std_logic;
begin
  -- Comments -----
  U1: notgate port map(a, inva);
  U2: notgate port map(b, invb);
  U3: notgate port map (c, invc);
  -- Now we can drive outputs ----
  U4: nandgate port map(inva, invb, invc, d0);
  U5: nandgate port map(a, invb, invc, d1);
  U6: nandgate port map(inva, b, invc, d2);
  U7: nandgate port map(a, b, invc, d3);
  U8: nandgate port map(inva, invb, c, d4);
  U9: nandgate port map(a, invb, c, d5);
  U10: nandgate port map(inva, b, c, d6);
  U11: nandgate port map(a, b, c, d7);
end tentti_arch;

```